

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, January 2013
Electrical and Electronic Measurements and Instrumentation

Time: 3 hrs.

Max. Marks: 100

**Note: Answer FIVE full questions, selecting
at least TWO questions from each part.**

PART – A

1.
 - a. Obtain the dimensional equations for resisting and conductivity in S.I. Units. (04 Marks)
 - b. Explain with neat sketch how megger is used for the measurement of very high resistance. (06 Marks)
 - c. Obtain wheatstone bridge sensitivity in terms of the parameters of the bridge. (10 Marks)
2.
 - a. Explain how capacitance and dissipation factor is measured using Schering bridge. (07 Marks)
 - b. Explain how Anderson's bridge used for measurement of inductance of the coil. (08 Marks)
 - c. The four arms of AC bridge are as: Arm AB: An insulating material representing an imperfect capacitor, Arm BC: a non inductive resistance of $1200\ \Omega$, Arm DA: a loss free capacitor of $100\ \mu\text{F}$, Arm CD: A resistance $300\ \Omega$ in parallel with capacitance of $0.6\ \mu\text{F}$. An AC supply of 50 Hz is connected across AC and detector is connected across BD. Determine capacitance, equivalent series resistance and loss angle of insulating material. (05 Marks)
3.
 - a. Explain construction of CT and PT with their necessary phasors. (10 Marks)
 - b. A wattmeter has resistance of current coil and resistance of potential coil as $0.1\ \Omega$ and $6500\ \Omega$ respectively. Determine percentage error due to resistance only, when reading of input to an apparatus which takes, i) 12 Amps at 250 volts with 4 pf ii) 12 Amps, 250 volts with 0.4 pf. (10 Marks)
4.
 - a. With neat sketch explain construction and operating principle of induction type energy meter. (10 Marks)
 - b. Explain how 3- ϕ reactive power is measured. (05 Marks)
 - c. A 250 volts, 1- ϕ energy meter has constant load of 6 Amps passing through it for 8 hours at 0.75 pf. If the disc makes 3200 revolution during this period, what is the energy meter constant in revolutions/kilowatt hour? Calculate the power factor of the load, if the number of revolutions made by energy meter is 600, when operating at 250 volts, 6 Amps for 2 hours. (05 Marks)

PART – B

5.
 - a. With necessary sketches, explain the construction and operating principle of 1- ϕ power factor meter. (08 Marks)
 - b. Explain with neat figure TRUE RMS responding meter. (06 Marks)
 - c. Compute the value of distributed capacitance of a coil when the following measurements were made. At frequency $f_1 = 2\ \text{MHz}$, the tuning capacitor is set at 450 PF. When the frequency is increased to 5 MHz, the tuning capacitor is tuned at 60 PF. (06 Marks)
6.
 - a. Classify the transducers with an example. (04 Marks)
 - b. Explain construction and operating principle of LVDT with necessary sketches. (10 Marks)
 - c. List out the temperature detectors. Explain resistance temperature detector. (06 Marks)

- 7 a. What do you mean by DAS (Data Acquisition System)? Explain with the block diagram digital DAS. (08 Marks)
b. Why recorders are necessary? Explain X-Y recorder with neat diagram. (08 Marks)
c. Write a short note on LED and Nixie tube. (04 Marks)
- 8 Write a short notes on the following:
a. Weston frequency meter.
b. Ramp type DVM.
c. Types of strain gauges.
d. Photoconductive cells. (20 Marks)

* * * * *