

USN

--	--	--	--	--	--	--	--	--	--

10ES33

Third Semester B.E. Degree Examination, June 2012
Logic Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1 a. Define combinational logic. List the various steps in designing a combinational logic system. (04 Marks)
- b. Define the following:
 - i) Literal
 - ii) Product of sums
 - iii) Canonical products of sums
 - iv) Sum of min-terms
 - v) Essential prime implicant.
- c. Simplify the function using K-Map:
 $y = f(a, b, c, d) = \sum m(0, 4, 5, 7, 8, 9, 11, 12, 13, 15)$. Write the simplified SOP and POS expression. (06 Marks)
- d. Design a 4-bit odd parity detector circuit and realize it using only NAND gates. (05 Marks)
- 2 a. Simplify the following using Q-M method. Use decimal notations:
 $f(a, b, c, d) = \sum (7, 9, 12, 13, 14, 15) + \sum d(4, 11)$. Realize the simplified expression using only NOR gates. (10 Marks)
- b. Determine minimal sum and minimal product using MEV technique, taking a, b and c as the map variables.
 $f(a, b, c, d) = \sum (3, 4, 5, 7, 8, 11, 12, 13, 15)$. Realize the simplified expression using only NAND gates. (10 Marks)
- 3 a. Design a combinational circuit to find the 9's complement of a single digit BCD number. Realize the circuit using suitable logic gates. (08 Marks)
- b. Implement the following function pairs using 74138 decoder:
 $f_1(a, b, c) = \sum(0, 2, 4)$; $f_2(a, b, c) = \sum(1, 2, 4, 5, 7)$. (06 Marks)
- c. Realize 16:4 encoder using two 8:3 priority encoders. (06 Marks)
- 4 a. Implement $f(a, b, c) = \sum(1, 4, 5, 7)$ using 4:1 multiplexer. (06 Marks)
- b. Design a suitable BCD adder circuit using 7483 and provision has to be made for self correction in case if the sum is not a valid BCD number. Justify your design with examples. (08 Marks)
- c. Design a 1-bit comparator using 2:4 decoder. Also design the circuit using only NOR gates. (06 Marks)

PART - B

- 5 a. Differentiate sequential logic circuit and combinational logic circuit. (04 Marks)
- b. What is the difference between latch and flipflop? Explain the operation of SR latch with an example. (06 Marks)
- c. Draw the circuit diagram of master slave JK flip flop using only NAND gates. Explain how race around condition is eliminated in this design. (06 Marks)
- d. Write a note on 0s and 1s catching problem. (04 Marks)
- 6 a. Derive the characteristic equations of SR, JK, D and T flipflops. (08 Marks)

1 of 2

10ES33

- b. Design mod-11 asynchronous counter using JK flipflops. (06 Marks)
- c. Design a 4 bit register using positive edge triggered D flipflops to operator as indicated in the table below--

Mode select	Register operation
$a_1 a_0$	
0 0	Hold
0 1	Clear
1 0	Complement contents
1 1	Circular right shift

Table 6(c)

(06 Marks)

- 7 a. With a suitable example explain Mealy and Moore model in a sequential circuit analysis. (10 Marks)
- b. A sequential circuit has one input and one output. The state diagram is as shown below in Fig.Q7(b). Design a sequential circuit using D-flipflop. (10 Marks)

 


Fig. Q7(b)

- 8 a. Design a counter using JK flipflops whose sequence is {0, 1, 4, 6, 7, 5, 0} by obtaining minimal sum equations. (10 Marks)
- b. Design a synchronous 5421 code sequence using positive edge triggered D-flipflop with minimum combinational circuits. (10 Marks)

2 of 2