

USN

--	--	--	--	--	--	--	--	--	--

10EE662

Sixth Semester B.E. Degree Examination, Dec.2015/Jan.2016
Advanced Power Electronics

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting atleast TWO questions from each part.

PART - A

1. a. With neat circuit diagram and waveforms, explain the operation of boost converter for continuous current conduction mode. (10 Marks)
 b. The buck dc – dc converter has the following parameters :
 $V_S = 50V$, $D = 0.4$, $L = 400\mu H$, $C = 100\mu F$, $f = 20KHz$, $R = 20\Omega$. Assuming ideal components, calculate i) The output voltage ii) The maximum and minimum inductor current and iii) The output ripple voltage. (10 Marks)
2. a. With neat circuit diagram and waveforms, explain the operation of cuk converter. (10 Marks)
 b. The buck – boost regulator has an input voltage of $V_S = 12V$. the duty cycle $K = 0.25$ and the switching frequency is $25KHz$. The inductance $L = 150\mu H$ and filter capacitance $C = 220\mu F$. The average load current $I_a = 1.25A$. Determine i) The average output voltage V_a ii) The peak to peak output ripple voltage ΔV_C iii) The peak to peak ripple current of inductor ΔI_L and iv) The peak current of the transistor I_P . (10 Marks)
3. a. With neat circuit diagram and waveforms, explain the working of single phase full bridge inverter. (10 Marks)
 b. With the help of neat circuit diagram and waveforms, explain square wave operation in three phase inverters. (10 Marks)
4. a. With the help of neat circuit diagram and waveforms, explain the basic concept of switch mode inverter and PWM switching scheme. (10 Marks)
 b. With neat circuit diagram and pwm waveforms, explain the operation of three phase voltage source inverter. (10 Marks)

PART - B

5. a. With neat circuit diagram and waveforms, explain the operation of zero current switching (ZCS) resonant switch converter. (10 Marks)
 b. With neat circuit diagrams, explain the working of parallel loaded resonant dc – dc converter. (10 Marks)
6. a. Mention the different steps to design a high frequency transformer. (10 Marks)
 b. What are the factors to be considered while designing the inductor? (10 Marks)
7. a. With a neat block diagram, explain the working of a switch mode dc power supply. (10 Marks)
 b. With neat circuit diagrams and waveforms, explain the operation of Flyback converter. (10 Marks)
8. a. With neat circuit diagram and waveforms, explain the operation of push – pull converter. (10 Marks)
 b. With neat circuit diagram, explain the working of switched mode ac power supplies. (10 Marks)
