

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, Dec.2014/Jan.2015

Logic Design

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

- 1 a. Design a combinational circuit which takes two, 2 – bit binary numbers as its input and generates an output equal to 1, when the sum of the two numbers is odd. (06 Marks)
- b. Convert the given Boolean function into :
 - i) $R = f(a, b, c) = (\bar{a} + b)(b + \bar{c})$ minterm canonical form
 - ii) $P = f(x, y, z) = x + x\bar{z}(y + \bar{z})$ maxterm canonical form. (06 Marks)
- c. Distinguish prime implicant and essential prime implicant. Determine PI and EPI for the given function $N = f(a, b, c, d) = \pi(0, 1, 4, 5, 8, 9, 11) + d(2, 10)$. Simplify the given function and implement using logic gates. (08 Marks)
- 2 a. Simplify the given Boolean function using Quine – Mccluskey method :
 $Y = f(a, b, c, d) = \Sigma(0, 1, 2, 6, 7, 9, 10, 12) + d(3, 5)$. Verify the result using k-map. (10 Marks)
- b. Find the minimal sum and minimal product for the given Boolean function, using MEV technique : Solve by using 3-variable map and 2 – variable map $y = f(a, b, c, d) = \Sigma(2, 3, 4, 5, 13, 15) + d(8, 9, 10, 11)$. (10 Marks)
- 3 a. Distinguish between a decoder and an encoder. Implement full adder using IC 74138. (08 Marks)
- b. Implement 3 – bit binary to gray code conversion by using IC 74139. (06 Marks)
- c. Design a priority encoder for a system with a 3 inputs, the middle bit with highest priority encoding to 10, the MSB with next priority encoding to 11, while the LSB with least priority encoding to 01. (06 Marks)
- 4 a. Realize the following Boolean function : $P = f(w, x, y, z) = \Sigma(0, 1, 5, 6, 7, 10, 15)$ using :
 i) 16 to 1 MUX ii) 8 : 1 MUX iii) 4 : 1 MUX. (10 Marks)
- b. With a neat logic diagram, explain carry look ahead adder. (10 Marks)

PART – B

- 5 a. Explain the working of a master –slave SR flip-flop with the help of a logic diagram, function table, logic symbol and timing diagram. (10 Marks)
- b. With a neat logic diagram, explain the working of positive edge triggered D flip-flop. (10 Marks)
- 6 a. Obtain the characteristic equation for D and T flip-flop. (06 Marks)
- b. With a neat logic diagram, explain the operation of 4-bit SISO unidirectional shift register. (06 Marks)
- c. Explain the working of four-bit binary ripple up counter, configured using positive edge triggered flip-flop. Also draw the timing diagram. (08 Marks)

- 7 a. Design synchronous mod-6 counter using D flip-flop to generate the sequence 0, 2, 3, 6, 5, 1, 0 (10 Marks)
- b. Compare Mealy and Moore sequential circuit models. (04 Marks)
- c. Analyze the sequential circuit shown in Fig. Q7(c). (06 Marks)

 


Fig. Q7(c)

Write input and output equations, transition table, state table and state diagram.

- 8 a. Write the basic recommended steps for the design of a clocked synchronous sequential circuit. (06 Marks)
- b. Compare synchronous and asynchronous counter. (04 Marks)
- c. A sequential circuit has one input and one output. The state diagram is as shown in the Fig. Q8(c). Design the sequential circuit with J-K flip-flop. (10 Marks)

 


Fig. Q8(c)

* * * * *