

--	--	--	--	--	--	--	--	--	--

Fifth Semester B.E. Degree Examination, May 2017

Linear IC's and Applications

Time: 3 hrs.

Max. Marks:100

Note: 1. Answer any FIVE full questions, selecting atleast TWO questions from each part.

2. Use of resistor, capacitor standard values list/data sheets are permitted.

PART – A

- 1
 - a. A capacitor coupled voltage follower is to be designed to have a lower cut-off frequency of 120 Hz. The load resistance is $8.2\text{ k}\Omega$ and the op-amp used has a maximum input bias current of 600 nA. Design a suitable circuit. (05 Marks)
 - b. Sketch the capacitor coupled difference amplifier and derive the equation for output voltage. (08 Marks)
 - c. Show how a capacitor coupled non-inverting amplifier should be connected to use a single polarity supply. Explain. (07 Marks)
- 2
 - a. Discuss the operational amplifier circuit stability and show how feedback in an inverting amplifier can produce instability. (08 Marks)
 - b. Sketch and explain a circuit to show Z_{in} mod method of frequency compensation. (07 Marks)
 - c. List the precautions that should be observed for operational amplifier circuit stability. (05 Marks)
- 3
 - a. Design a precision full-wave rectifier consists of half wave rectifier and summer to produce 2V peak output from a sine wave input with a peak value of 0.5 volts and a frequency of 1 MHz. Use 741 op-amp with a supply of $\pm 15\text{V}$. (06 Marks)
 - b. With a neat circuit diagram and waveforms explain the working of precision peak detector. (07 Marks)
 - c. With a neat circuit diagram explain the operation of precision clamping circuit. (07 Marks)
- 4
 - a. With circuit diagram and waveforms, explain the operation of inverting Schmitt trigger circuit and show input/output characteristics. (07 Marks)
 - b. Design an astable multivibrator to generate a square wave signal with an amplitude of $\pm 14\text{V}$, using 741 op-amp. The signal frequency is to be 3 kHz. (06 Marks)
 - c. With neat circuit diagram and relevant waveforms explain the operation of monostable multivibrator. (07 Marks)

PART – B

- 5
 - a. With a neat circuit diagram and waveforms explain the operation of triangular/rectangular wave generator. Show the arrangement to adjust frequency and duty cycle of output signal. (10 Marks)
 - b. Draw the circuit of RC phase shift oscillator using op-amp. Explain how Barkhausen conditions are satisfied and output amplitude can be stabilized. (10 Marks)

- 6** a. With frequency response, explain first order high pass filter. **(06 Marks)**
b. Design a second order low pass filter to have a cutoff frequency of 1 kHz using 741 op-amp. **(04 Marks)**
c. Explain the principle of Band pass filter with its frequency response and show the design equations. **(10 Marks)**
- 7** a. What is phased locked loop? Explain the working of phase locked loop with neat block diagram. **(08 Marks)**
b. Write a short notes on:
(i) Universal Active Filter
(ii) Power Amplifiers. **(12 Marks)**
- 8** a. Define the terms line regulation and load regulation for a d.c. voltage regulator. **(04 Marks)**
b. Explain the operation of series op-amp regulator with neat circuit diagram. **(06 Marks)**
c. Show the basic circuit of a 723 I.C. Regulator and explain its operation. What are its special features? **(10 Marks)**

* * * * *