

--	--	--	--	--	--	--	--	--	--

Sixth Semester B.E. Degree Examination, Dec.2017/Jan.2018
Advanced Power Electronics

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

- 1 a. With a neat circuit and wave form, explain the operation of 'CUK' – converter. Find the ratio of output current to input current. (10 Marks)
- b. A Boost regulator has an input voltage of $V_s = 5V$. The average output voltage is $V_a = 15V$ and the average load current $I_a = 0.5A$. The switching frequency is 25 KHz. If $L = 150 \times 10^{-6}H$ and $C = 220 \times 10^{-6}F$, determine :
 i) The duty cycle(k), ii) the ripple current of inductor iii) the peak current of inductor iv) the output ripple voltage. (10 Marks)
- 2 a. Discuss the working of Boost converter for continuous conduction mode with the help of circuit diagram and relevant waveforms. Also derive its voltage and current transformation ratio. (10 Marks)
- b. The buck DC-DC converter has the following parameters $V_s = 50V$, $D = 0.4$, $L = 400 \times 10^{-6}H$, $C = 100 \times 10^{-6}F$, $f = 20$ KHz, $R = 20\Omega$. Assuming ideal components, calculate : i) the output voltage ii) the maximum inductor current iii) the minimum inductor current and iv) the output voltage ripple. (10 Marks)
- 3 a. Describe the working of buck-boost converter for continuous conduction mode with the help of relevant circuit and waveforms. Also derive voltage and current transformation ratio in terms of duty cycle. (10 Marks)
- b. The Buck – Boost regulator has an input voltage of $V_s = 12V$ the duty cycle $K = 0.25$ and the switching frequency is 25 KHz the inductance $L = 150 \times 10^{-6}H$ and the filter capacitance $C = 220 \times 10^{-6}F$. The average load current $I_a = 1.25A$. Determine :
 i) The average output voltage (V_0)
 ii) Peak – to – peak output voltage ripple (ΔV_0)
 iii) Peak – to – peak ripple inductor current (ΔI_L)
 iv) Peak current of transistor (I_p). (10 Marks)
- 4 a. With a neat circuits, explain the operations of single phase half bridge and full bridge inverters. (10 Marks)
- b. Explain the operation of three phase inverter consisting of three legs. (05 Marks)
- c. In a single phase full-bridge PWM inverter, V_d varies in a range of 295 – 325V. The output voltage is required to be constant at 200V(rms) and the maximum load current is 10A(rms). Calculate the combined switch utilization ratio. (05 Marks)

PART – B

- 5 a. With a neat snubber circuit and switching loci, explain the operation of zero voltage and zero current switchings. (10 Marks)
- b. Explain different modes of operation of zero voltage switching (ZVS) resonant switch converter with relevant circuits and waveforms. (10 Marks)

- 6 a. Explain the step by single pass algorithm for the design of high frequency inductor. (10 Marks)
b. Give the steps involved in single pass algorithm for the design of high frequency transformer used with SMPS. (10 Marks)
- 7 a. Explain the operation of push-pull converter with relevant circuit and waveform. Also derive its voltage transformation ratio in terms of duty cycle. (10 Marks)
b. Explain the operation of full bridge DC – DC converter with neat circuit and waveform. (10 Marks)
- 8 a. Derive the voltage and current transformation ratio for a flyback converter with the help of neat circuit and waveforms. (10 Marks)
b. What are the types of AC power supplies? With a block diagram clearly. Explain 'UPS' configuration with load normally connected to AC main supply. (10 Marks)

* * * * *