USN												10ELE15/25
-----	--	--	--	--	--	--	--	--	--	--	--	------------

First/Second Semester B.E. Degree Examination, June/July 2018 Basic Electrical Engineering

Time: 3 hrs. Max. Marks:100

Note: Answer any FIVE full questions, choosing at least two from each part.

TANI - A

- 1 a. Choose the correct answers for the following:


 i) The equivalent resistance of two branch parallel circuit will be
 - A) Higher than greatest R
- B) Smaller than smallest R

C) Equal to any one R

- D) None of these
- ii) Branch current division method is Applicable to _
 - A) Two
- B) One
- C) Three
- D) Four
- iii) According to Law, the induced EMF opposite the cause producing it
 - A) Ohm's
- B) Faraday's law
- C) Lenz's
- D) Kirchhott's law

- iv) The self inductance is the property of _
 - A) Conductor
- B) Coil
- C) Insulator
- D) None of these
- b. State and explain Faraday's law of Electromagnetic Induction.
- (05 Marks)
- c. For the circuit shown in fig.Q1(c), calculate the value of the current in either branch and the value of unknown resistance 'R'. When the total current taken by the circuit is 2.25A.

(06 Marks)

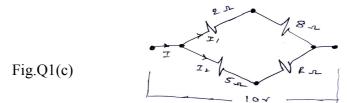

- d. A coil consists of 750 turns. A current of 10A in the coil gives rise to a magnetic flux of 1200 μ wb. Determine the inductance of the coil and the average EMF induced in the coil when this current is reversed in 10ms. Also find the energy stored in inductance. (05 Marks)
- a. Choose the correct answers for the following:

(04 Marks)

- i) Power consumed by a pure inductive circuit is
 - A) Zero
- B) Infinity
- Non zero
- D) None of these
- ii) Peak value of a sine wave is 400V. its average value is
 - A) 565.5V
- B) 282.6V
- C) 400V
- D) 254.6V
- iii) In a R L series circuit, $V_R = 8V & V_L = 6V$. The magnitude of total voltage is
 - A) 8V
- B) 6V
- C) 10V
- D) 5V

- iv) As the p.f. increases, phase angle
 - A) Decreases
- B) Increases
- C) Remains same
- D) None of these
- b. Show that average power consumed in a pure resistive circuit is never zero. (05 Marks)
- c. A coil of power factor 0.6 is in series with a 100µf capacitance. When connected to a 50Hz supply, the potential difference across the coil is equal to the potential difference across the capacitance. Find the resistance and inductance of the coil. (06 Marks)
- d. Two impedances $(20 + j15) \Omega$ and $(30 j20) \Omega$ are connected in parallel. Find the branch currents if the total current is $\angle -30^{0}$ A. Draw the vector diagram. (05 Marks)

(06 Marks)

3	a.	a. Choose the correct answers for the following:		(04 Marks)							
		i) Algebric sum of all the phase voltages at any time in	a3 – phase balanced syste	em is							
		A) zero B) one C) infi									
		ii) For the same rating, the size of a $3 - \phi$ machine is	that of $1 - \phi$ machine								
		A) more than B) same as C) less		these							
		iii) In the measurement of $3 - \phi$ power by 2 wattame									
		reads zero, then the p.f of the circuit is									
			ween 0 and 1 D) 0.5								
		iv) The total apparent power in a 3 – \$\phi\$ system is given									
		A) $\sqrt{3}$ V _L I _L B) $\sqrt{3}$ V _L I _L cos ϕ C) $\sqrt{3}$	V I sin b D) V I								
	b.	b. Show that in 3 phase, star connected system, the line vol	= =	_							
				(05 Marks)							
	c.	c. A 3 phase, star connected supply with a phase voltage of									
		load. The load draws 15kw at 0.8 pf. lagging. Find circu		(06 Marks)							
	d.	d. During the measurement of power by two wattameter is									
		phase, 440V, motor running at a p.f of 0.8, was found	to be 25kw. Find the read	ings of the							
		two wattmeters.		(05 Marks)							
4	0	a. Choose the correct answers for the following:		(04 Marks)							
4	a.	7 / ****** =		(04 Marks)							
		i) A fuse is a P) Cum	mant limiting davias								
	.40.		rent limiting device	_ <							
			wer limiting device								
M /		ii) In a Dynamometer wattameter the fixed coil is	e: 1								
			ential coil								
		, ,	ne of these								
		iii) A good earthing should provideresistance in ea	orth path	A Proposition of the Contract							
		A) Low B) High C) Med	- 10 March 1981 1981 1981 1981 1981 1981 1981 198	fthese							
		iv) In energy meter, constant speed of Rotation of disc									
		A) Shunt magnet B) Series magnet C) Braki									
		b. Explain the construction and working of single phase inc	duction type energy meter.	(08 Marks)							
	c.	c. With neat sketch, explain plate earthing.		(04 Marks)							
	d.	d. Explain the factors affecting the selection of wiring.		(04 Marks)							
		<u>PART - B</u>									
5	•		\	(04 M1)							
3	a.	a. Choose the correct answers for the following:		(04 Marks)							
		i) Generator works on the principles of	Garatta In Assaul EME								
			tually Induced EMF								
			ne of these								
		ii) Number of parallel paths equal to the number of pole		0.1							
		· · · · · · · · · · · · · · · · · · ·	wave and lap D) None o	t these							
		iii) Generator is used for Battery charging.									
		A) DC series B) DC shunt C) Both series and shunt D) None of these									
		iv) Function of a starter in a DC motor is to									
		- \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \	crease starting torque								
		P 3 Name 1	one of these								
	b.	/ \ Y //		(05 Marks)							
	c.	e. A DC shunt generator supplying load of 5kw at a vo	oltage of 250V. If it has s	shunt field							
		resistance of 100Ω and armature resistance of 0.22Ω , ca	lculate generated EMF.	(05 Marks)							
	d.			` /							

resistance of 230Ω .

current is 41 Å, find the speed on full load. Take armature resistance of 0.25Ω and shunt field

				<u> </u>
			. 6	
				10ELE15/25
6	a.	Choose the correct answers for the following:		(04 Marks)
		i) A transformer is and device		
		A) Static and DC	B) Static and AC	
		, ,	D) Dynamic and DC	
		ii) Number of primary winding of a Transform		D) None of these
		A) Input voltage B) Input current iii) The frequency of secondary voltage is		D) None of these
			C) same as	
		iv) Losses which vary with load in a transform	,	D) None of these
			B) Copper loss	
			D) Frictional loss	
	b.	. What is Transformer? Derive an expression for i		(05 Marks)
		. A 50KVA, single phase transformer has 600 tur		turns on the secondary.
		The primary winding is connected to the 2200		alculate i) secondary
		voltage on no load ii) Full load primary & s		(05 Marks)
	d.	1. A single phase transformer working at 0.8p.f ha		
		& full load. Determine the efficiency at half of for	ull load and UPF.	(06 Marks)
7	a.	. Choose the correct answers for the following:		(04 Marks)
		i) In an alternatoris a rotating part		
			B) Armature system	_ <
			D) None of these	<i>(\lambda</i>)
Transfer of the same of the sa		Salient pole type rotor has diameter a		
	anna da	A) Larger, Larger B) Smaller, Smaller		D) Smaller (Larger
		iii) Field winding of an Alternator is excited by A) AC B) DC	C) Both AC & DC	D) None of these
		iv) Number of cycles generated in a 6 pole Alte		
		, , ,	C) 3	D(4)
	b.	. What are the advantages of rotating field synchro	onous generator?	(04 Marks)
	c.	Derive an expression for induced EMF equation	for a star connected	Alternator. (06 Marks)
	d.	. A 6 pole, 3 phase. Star connected Alternator has		
		/ slot. It rotates at 1000 rpm, the flux/phase being	ng 50mwb. Calculate	
		generated, if the $K_d = 0.96$ and $K_c = 0.97$.		(06 Marks)
8	a.	. Choose the correct answers for the following:		(04 Marks)
		i) An Induction motor works with supply		
		· · · · · · · · · · · · · · · · · · ·	C) Both DC & AC	D) None of these
		ii) Frame of Induction motor is usually made of	<u> </u>	
			C) Aluminum	D) Bronze
		iii) Stator winding of 3 – φ Induction motor prod	-	D) D + + +
		· · · · · · · · · · · · · · · · · · ·	C) Constant	D) Rotating
		iv) In Squirrel cage rotor, slots are skewed beca A) To reduce loss	use 3) To give support	
			(a) To give support (b) To reduce friction	
	h	b. Explain the construction of 3 phase Induction me	/	(06 Marks)
		Explain the working of 3 phase Induction motor		(05 Marks)
		I. A 3 phase Induction motor has 6 polar and run		
		from a Alternator having 4 poles and running a	_	
		frequency of induced EMF.		(05 Marks)