

## Third Semester B.E. Degree Examination, Jan./Feb. 2023

### Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

#### Module-1

- 1 a. Using source transformation and source shifting techniques, find voltage across  $2\Omega$  resistor in the Fig.Q1(a).

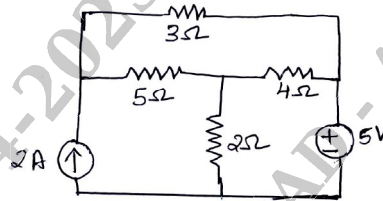


Fig.Q1(a)

(06 Marks)

- b. Using star delta transformation find equivalent resistance between AB in the Fig.Q1(b).

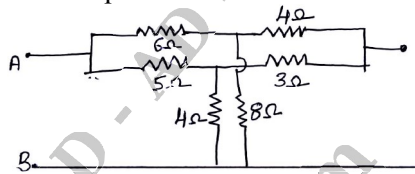


Fig.Q1(b)

(08 Marks)

- c. Use node analysis and find the value of  $V_x$  in the Fig.Q1(c) circuit such that the current through the impedance  $(2 + j3)\Omega$  is zero.

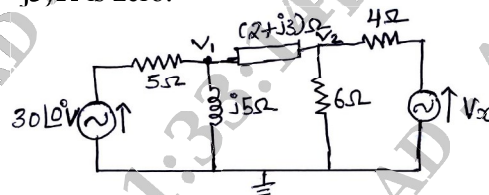


Fig.Q1(c)

(06 Marks)

#### OR

- 2 a. Find the loop currents  $I_1$ ,  $I_2$  and  $I_3$  in the circuit shown in Fig.Q2(a).

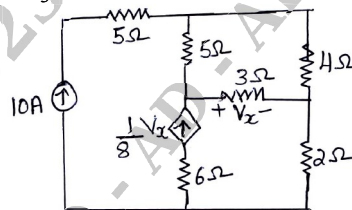


Fig.Q2(a)

(06 Marks)

- b. For the networks shown in Fig.Q2(b) find the node voltages  $V_d$  and  $V_c$ .

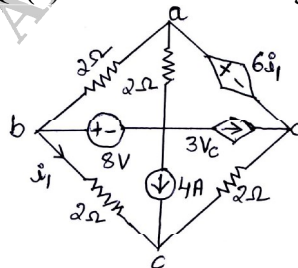


Fig.Q2(b)

(08 Marks)

- c. Explain with circuit diagram how to find loading effect of different voltmeter in an electric circuit.

(06 Marks)

**Module-2**

- 3 a. State and explain superposition theorem. (06 Marks)  
 b. Obtain the Thevenin's and Norton's equivalent circuits at terminals AB for network. Find the current through  $10\Omega$  resistor across AB in the Fig.Q3(b).

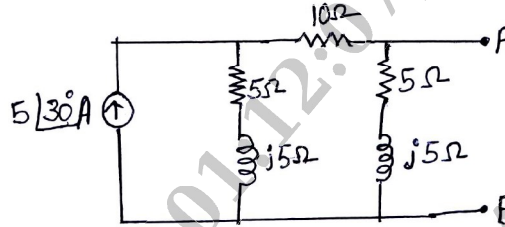


Fig.Q3(b)

(08 Marks)

- c. Using Millman's theorem, find  $I_L$  through  $R_L$  for the network shown in Fig.Q3(c).

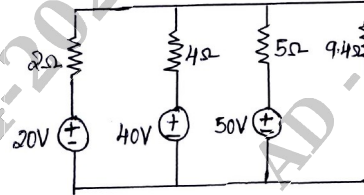


Fig.Q3(c)

(06 Marks)

**OR**

- 4 a. State and prove maximum power transfer theorem for AC network. (06 Marks)  
 b. Calculate  $i_x$  and verify reciprocity theorem for the Fig.Q4(b).

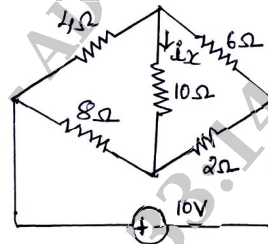


Fig.Q4(b)

(08 Marks)

- c. Find the Thevenin's equivalent of the network shown in Fig.Q4(c).

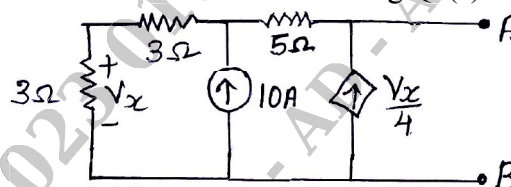


Fig.Q4(c)

(06 Marks)

**Module-3**

- 5 a. Explain parallel resonance. Derive the condition for parallel resonance when RL connected parallel to RC. (06 Marks)  
 b. Determine  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$  when the switch K is moved from position 1 to 2 at  $t = 0$  for the network shown in Fig.Q5(b). Assume capacitor is initially uncharged.

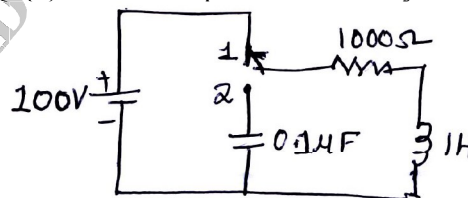


Fig.Q5(b)

(08 Marks)

- c. A series RLC circuit has  $R = 4\Omega$ ,  $L = 1\text{ mH}$  and  $C = 10\mu\text{F}$ . Calculate Q factor, bandwidth, resonant frequency and the half power frequencies  $f_1$  and  $f_2$ . (06 Marks)

OR

- 6 a. What are initial conditions? Show the behavior of R, L, C elements at the time of switching at  $t = 0$  both at  $t = 0^+$  and  $t = \infty$ . (06 Marks)
- b. In the network shown in Fig.Q6(b)  $V = 10\text{V}$ ,  $R = 10\Omega$ ,  $L = 1\text{H}$ ,  $C = 10\mu\text{F}$  and  $V_C(0) = 0$ . Find  $i(0^+)$ ,  $\frac{di}{dt}(0^+)$  and  $\frac{d^2i}{dt^2}(0^+)$ .

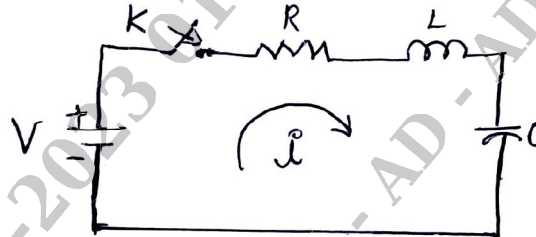


Fig.Q6(b)

(08 Marks)

- c. Derive the expression for quality factor (Q – factor) in a parallel resonant circuit. Explain its utility in comparing resonant circuits, selectivity. (06 Marks)

**Module-4**

- 7 a. State and prove initial and final value theorem. (08 Marks)
- b. Find the Laplace transform of the wave form shown in Fig.Q7(b).

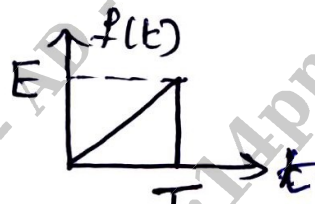


Fig.Q7(b)

(06 Marks)

- c. For the circuit shown Find an expression for  $i(t)$  when the switch K is closed at  $t = 0$ . Assume there is no initial charge on capacitor, shown in Fig.Q7(c).

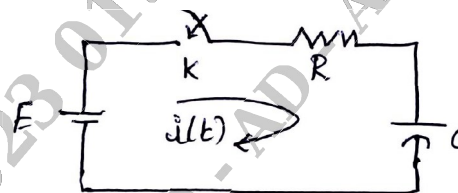


Fig.Q7(c)

(06 Marks)

OR

- 8 a. Find the Laplace transform of unit step, unit impulse and unit ramp functions. (06 Marks)
- b. Find initial and final values of following functions :  
 i)  $i(t) = 3e^{-t} - e^{-2t}$   
 ii)  $i(t) = 5u(t) - 3e^{-2t}$ . (06 Marks)
- c. Determine the Laplace transform of the periodic saw tooth waveform. Shown in Fig.Q8(c).

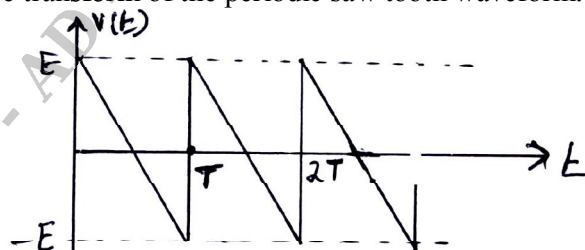


Fig.Q8(c)

(08 Marks)

**Module-5**

- 9 a. Define  $[Z]$  and  $[T]$  parameters and derive  $[Z]$  in terms of  $[T]$ . (06 Marks)  
 b. Find  $y$  parameters for the networks shown in Fig.Q9(b).

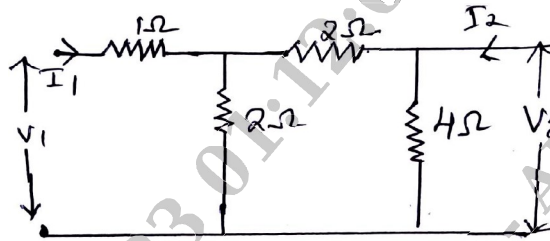


Fig.Q9(b)

- c. Derive the relationship between transmission and  $Z$  – parameters. (08 Marks)  
 (06 Marks)

**OR**

- 10 a. Find the  $Z$ -parameter of the circuit shown in Fig.Q10(a).

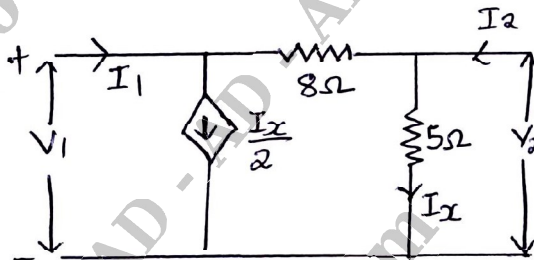


Fig.Q10(a)

- b. Determine the line currents and total power supplied to a delta connected load of  $Z_{AB} = 10 \angle 60^\circ$ ,  $Z_{BC} = 20 \angle 90^\circ$ , and  $Z_{CA} = 25 \angle 30^\circ$ . Assume a  $3\phi$  400V, ABC system shown in Fig.Q10(b). Draw phasor diagram also. (10 Marks)

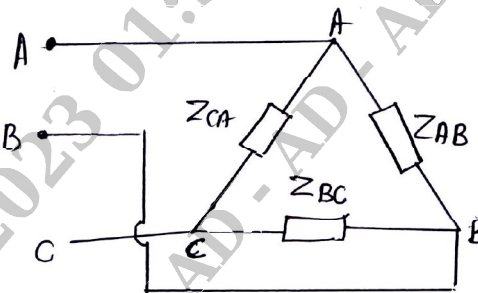


Fig.Q10(b)

(10 Marks)

\*\*\*\*\*